

Experiment 5

Combinational Logic Design

1. Design a 2 to 4 decoder with enable control and active low output.
2. Using the decoder in (1), design a 1 to 8 demultiplexer.