

## **Exercise 4**

1. Design an unsigned 3-bit magnitude comparator (including truth table and circuit diagram).

Simulate the same on Cadence Virtuoso.