

VLSI LAB Experiment-8 Transistor Layouts


Group Number: 2

Group Members:


Thathapudi Sanjeev Paul Joel - 2020AAPS0120H

Aditya Anirudh - 2020AAPS0373H

Schematic:

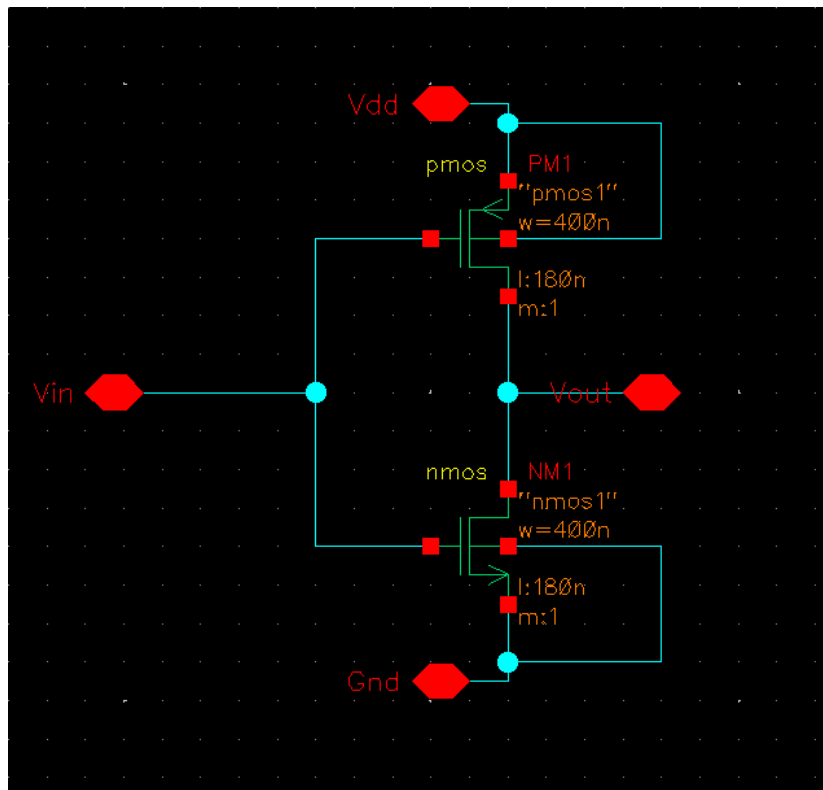


Layout:

 


Simulation Results:


Results obtained for DRC:-

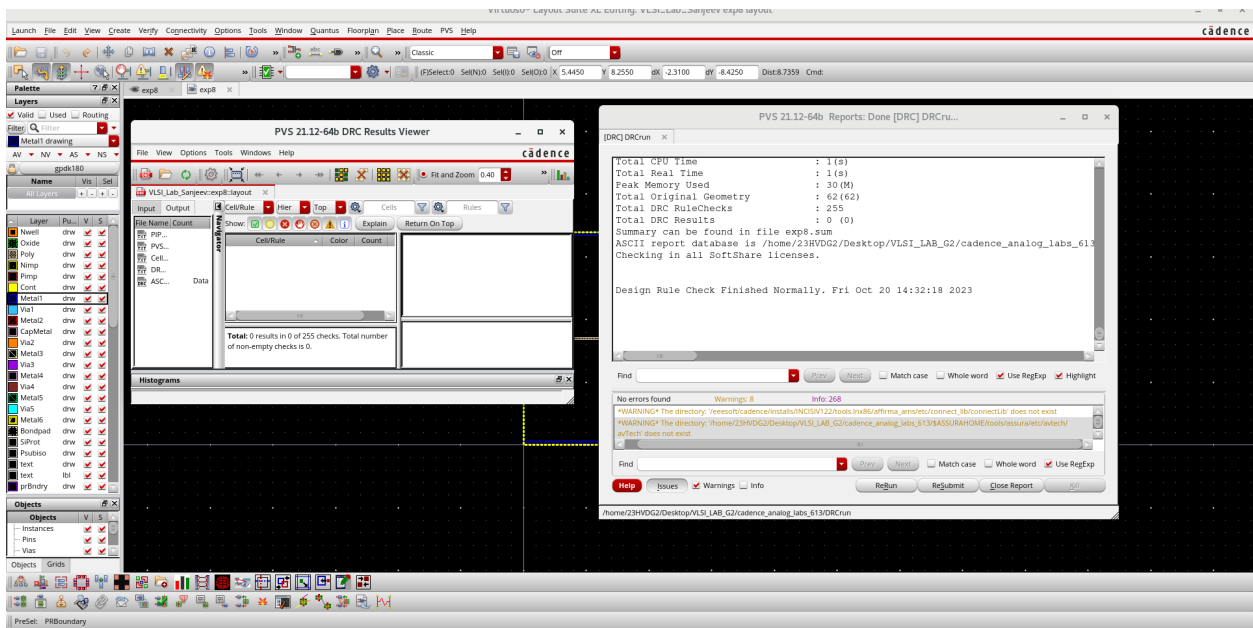

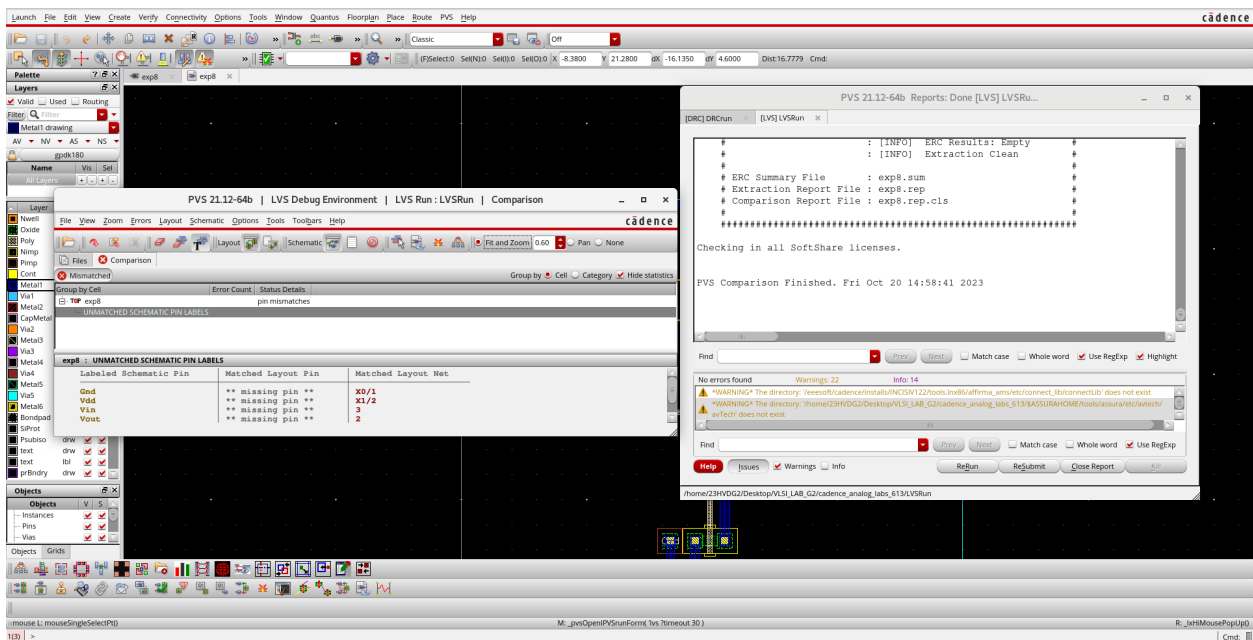Results obtained for LVS (before pin matching):-



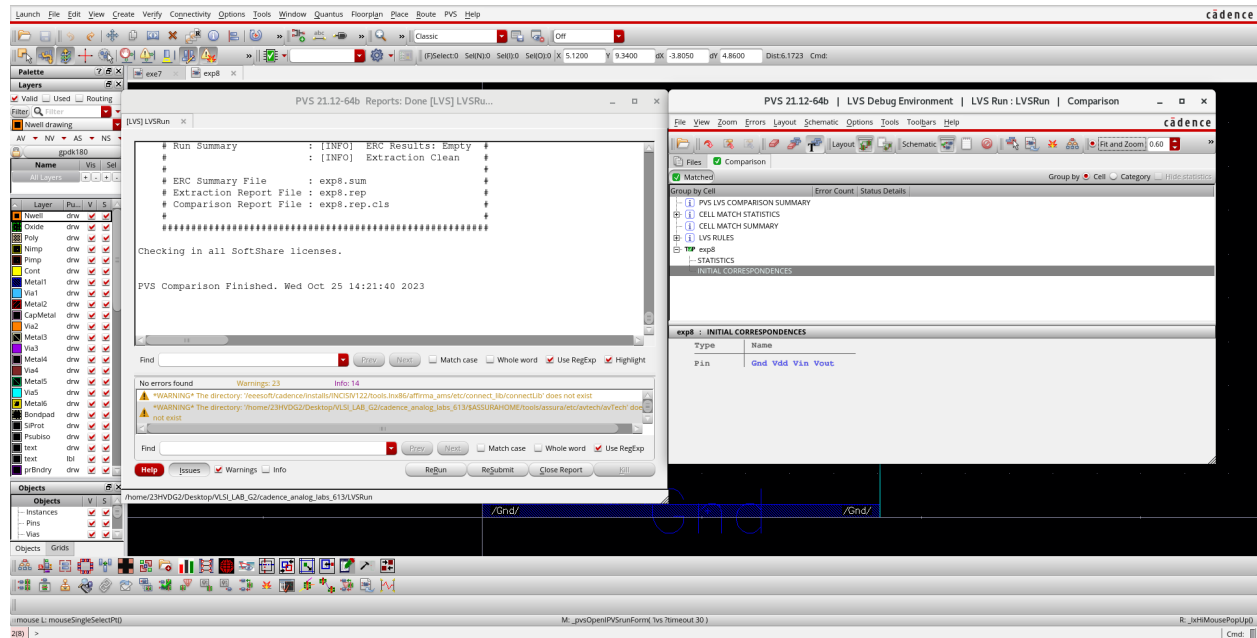Results obtained for LVS (after pin matching):-



Inferences:

1. We need to insert a **P-Substrate** and an **N-Well** intersecting with NMOS and PMOS transistors respectively to prevent **latchup effects**.
2. The above layout has been verified to be abiding by **DRC** and **LVS** rules.

Conclusion:

In this experiment, we learnt how to design the **layout for a CMOS Inverter** using Cadence. Then we used the **DRC** and **LVS** tools to check if the layout is behaving correctly or not.