

Exercise 5

1. Design an 8 to 1 multiplexer using NMOS-only Pass Transistor Logic.
2. Use a level restorer for achieving rail-to-rail voltage swing in (1). Comment on the impact of level restorer size on the performance (delay, power) and functionality of the circuit.