

VLSI LAB Experiment-5 Combinational Logic Circuits

Group Number: 2


Group Members:

Thathapudi Sanjeev Paul Joel - 2020AAPS0120H

Aditya Anirudh - 2020AAPS0373H

Schematics:

Decoder:-

 

Demux:-

Excitation Schematic:

Decoder:-

① 2:4 Decoder with active low output
and Enable Pin

Truth table:

E_n	I_1	I_0	O_0	O_1	O_2	O_3
0	x	x	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	1	1	1	0

From the truth table above, we can write the following logic equations




$$O_0 = \overline{(E_n \cdot \bar{I}_1 \cdot \bar{I}_0)}$$

$$O_2 = \overline{(E_n \cdot I_1 \cdot \bar{I}_0)}$$


$$O_1 = \overline{(E_n \cdot \bar{I}_1 \cdot I_0)}$$

$$O_3 = \overline{(E_n \cdot I_1 \cdot I_0)}$$



Design Schematic

   


Symbol

 


② 1:8 Demux

 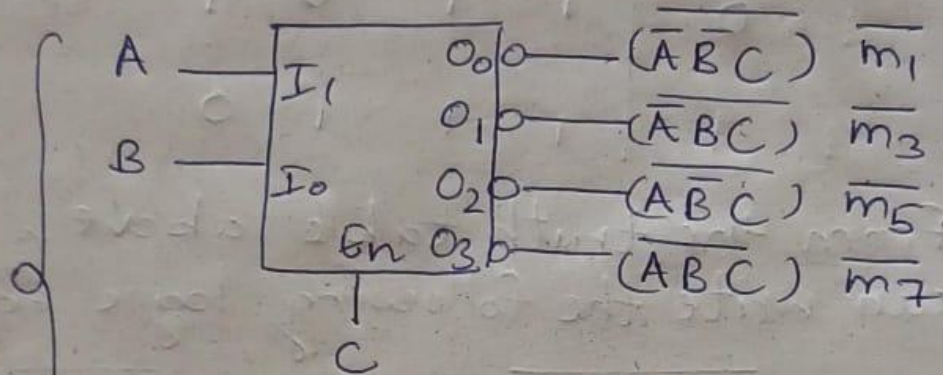

3:8 Decoder

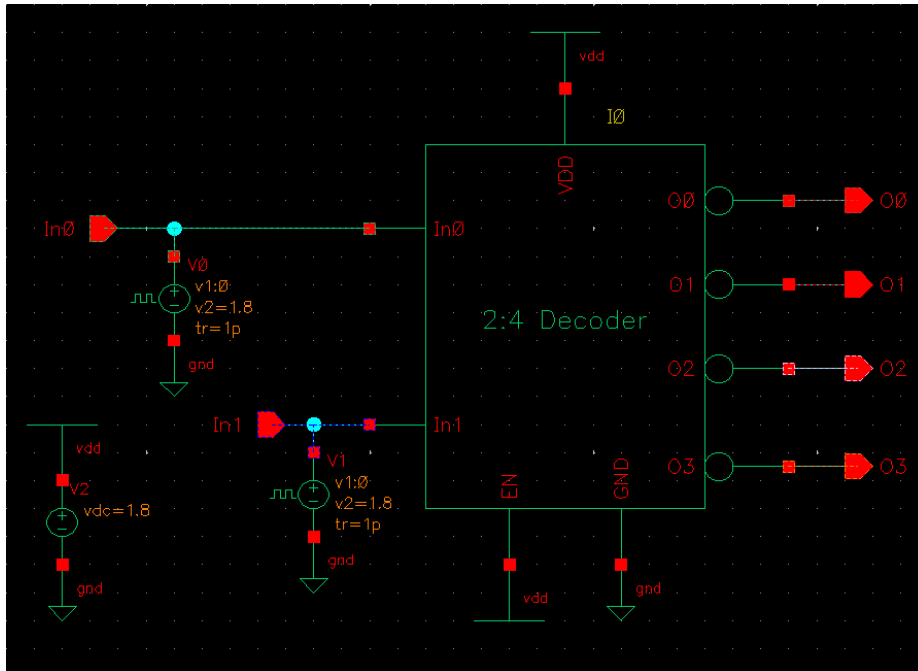


Demux:-

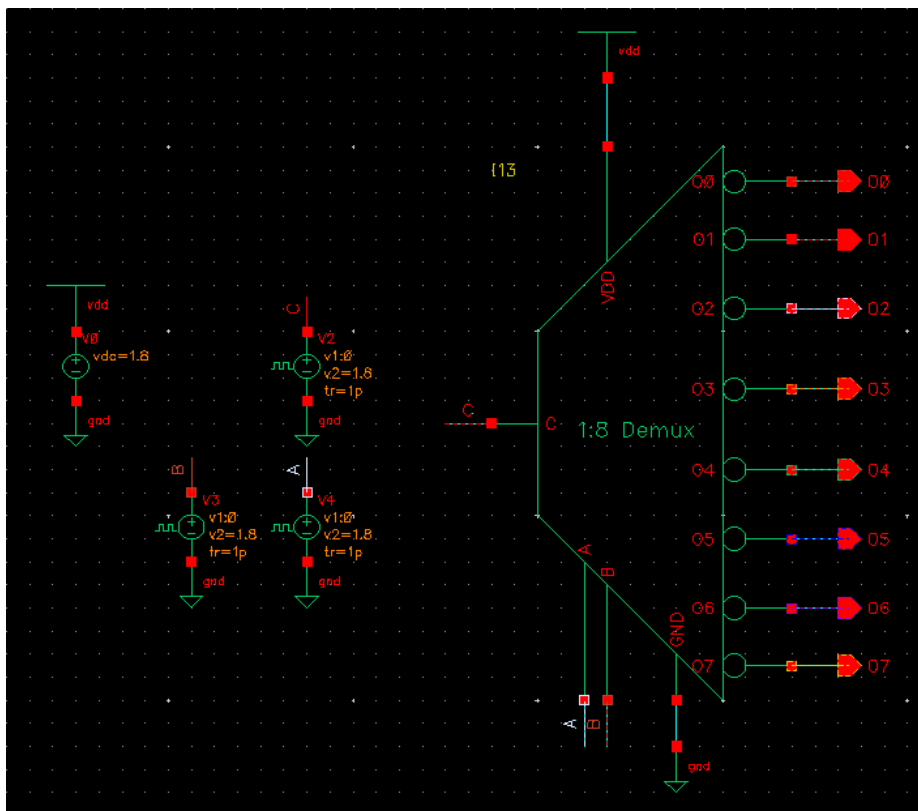


Waveforms:

Decoder:-

 

Demux:-

 

Conclusion:

In this experiment, we learnt how to design a 2:4 decoder using logic gates constructed in the previous experiment. Later by using the same decoder instance we designed a 1:8 demux in Cadence and simulated it for functional verification.