

VLSI LAB Exercise-3 STATIC CMOS LOGIC

Group Number: 2


Group Members:

Thathapudi Sanjeev Paul Joel - 2020AAPS0120H


Aditya Anirudh - 2020AAPS0373H

Schematics:

Schematic-1:

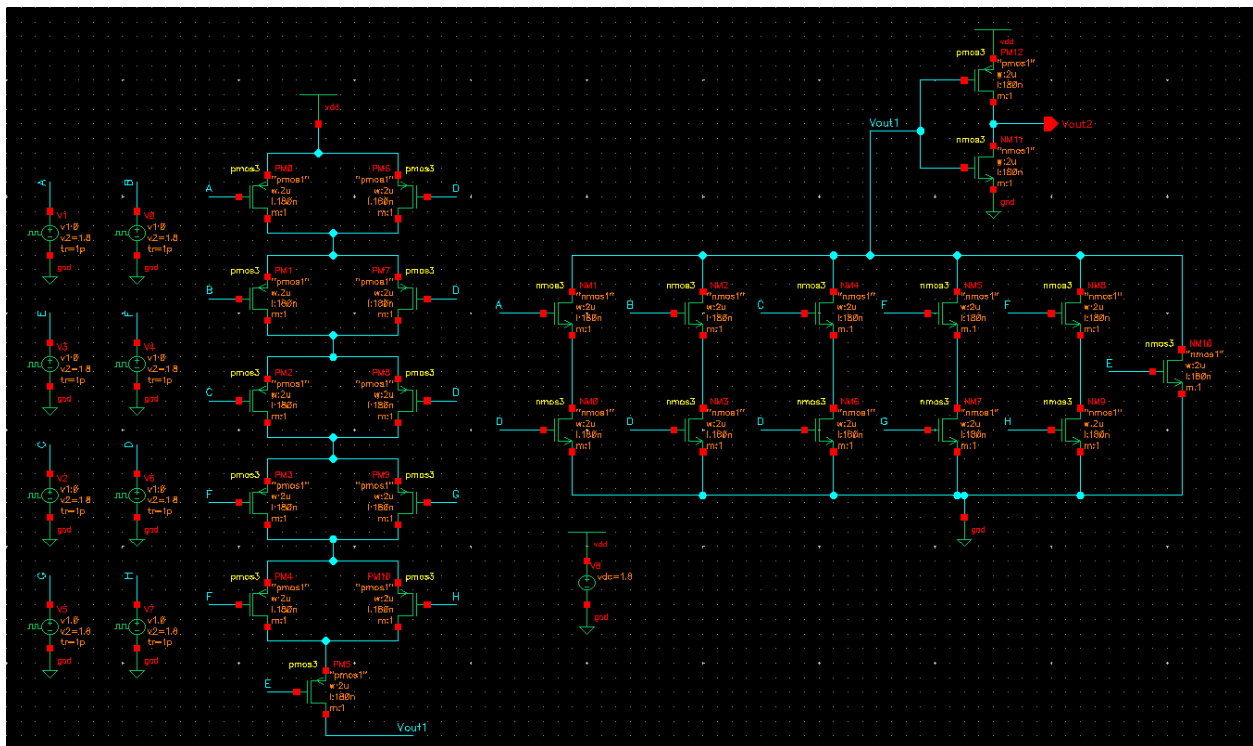

Schematic-2:

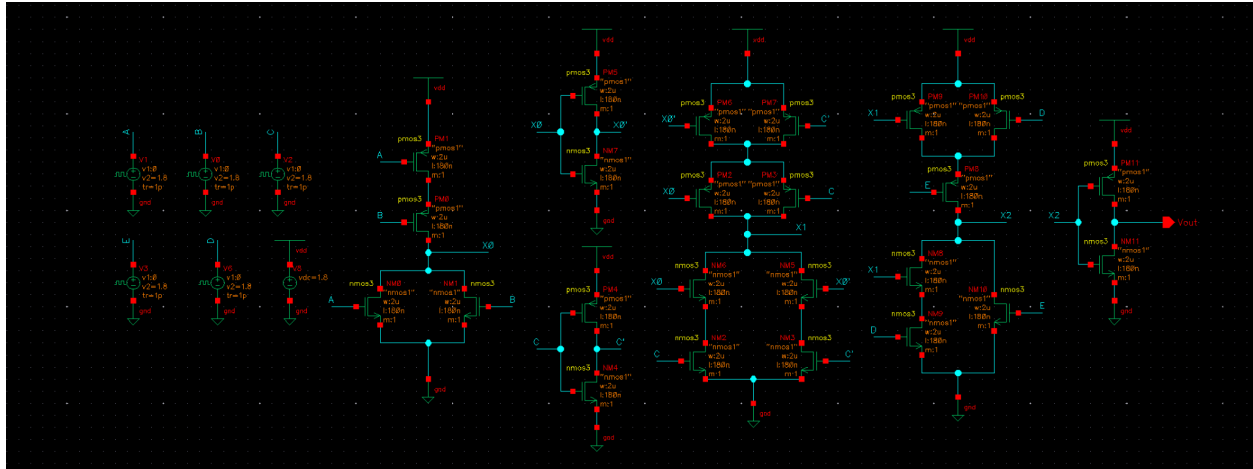

Design Workout:


11/09/23 Exercise - 3 STATIC CMOS CIRCUITS

1) (a) $Y = (A+B+C)D + E + F(G+H)$


$$\overline{Y} = \overline{[(A+B+C)D + E + F(G+H)]}$$

↓
We can write/design PDN for this function and then pass the result through an inverter to get the final output.

PDN -

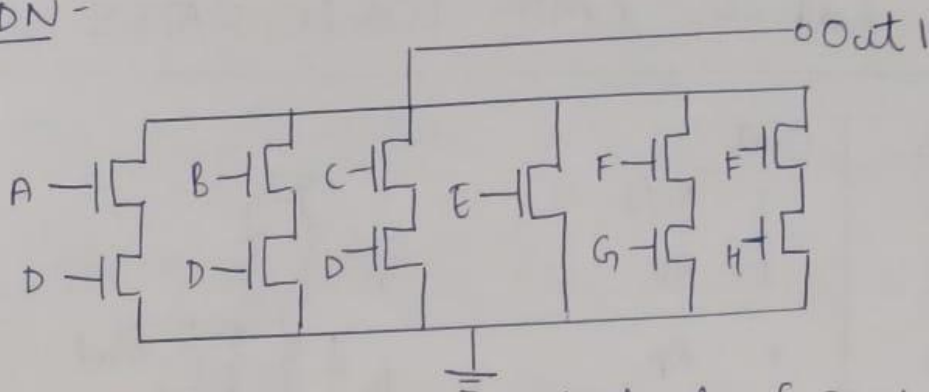

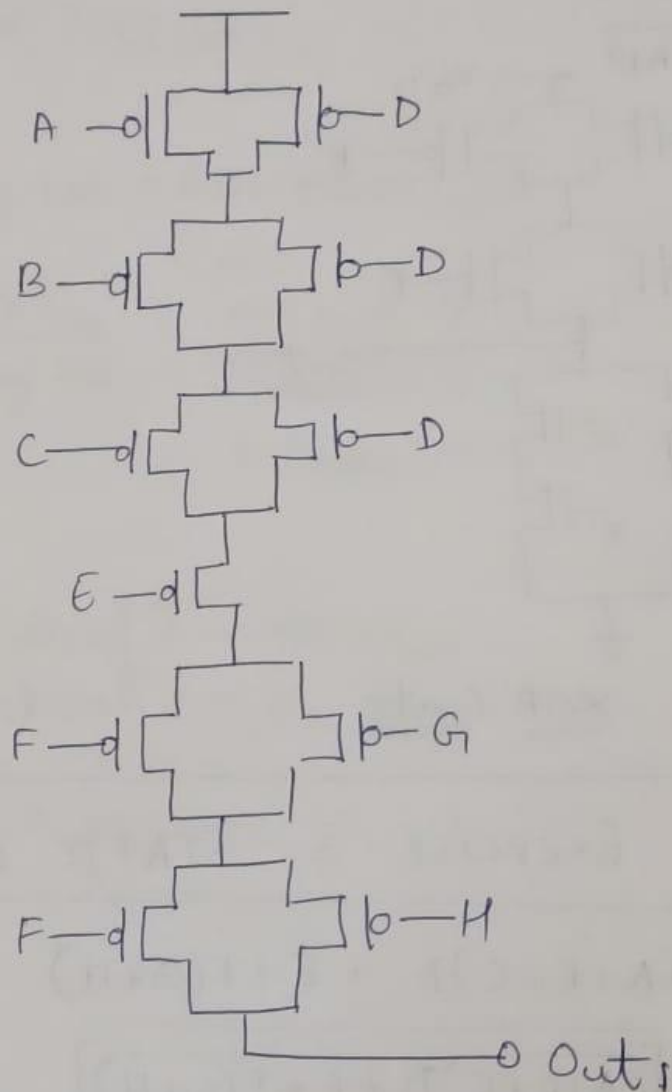The PUN will be the exact dual of PDN \Rightarrow



"Out1" drives the input of another inverter to get the final result.

$$(b) Z = (\overline{A+B} \wedge C)D + E$$

through an inverter to get the final output

$$\overline{(\overline{A+B} \wedge C)} D + E$$

Use NOR logic to implement this function



Then use the result & C values to pass them through an XOR logic

Then finally -

$$\overline{X_1 D + E}$$

Implement this using static CMOS Approach.

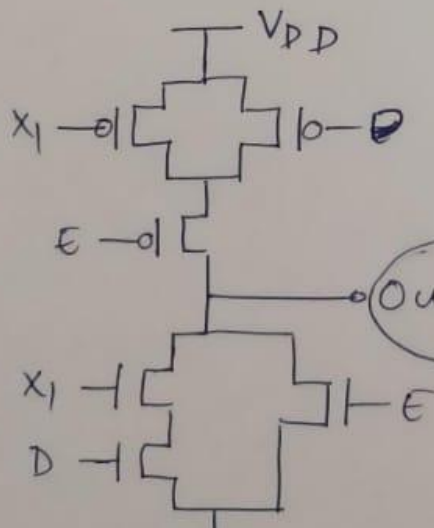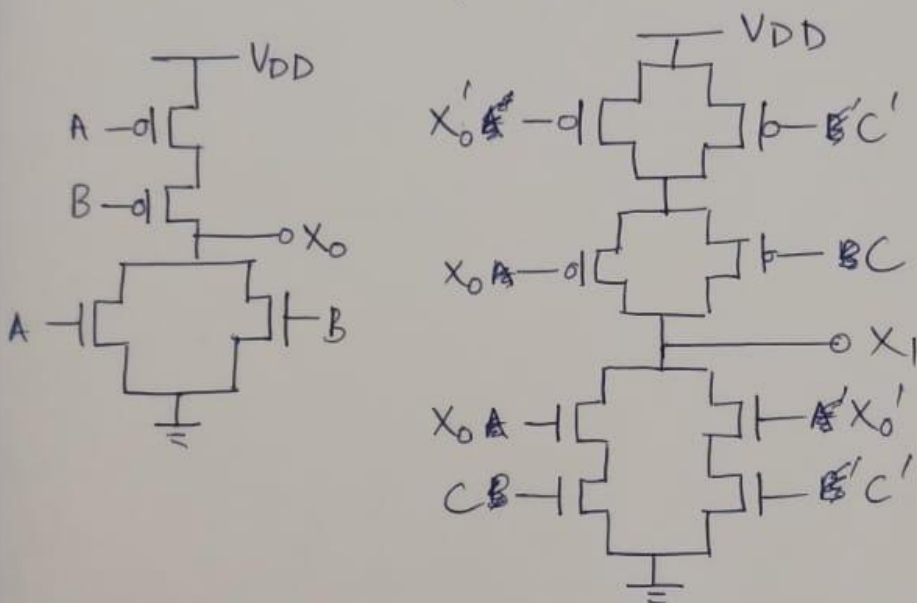
$$\text{where } X_1 = (\overline{A+B} \wedge C)$$




Drives another inverter to get the final result.

Waveforms:


Schematic-1:

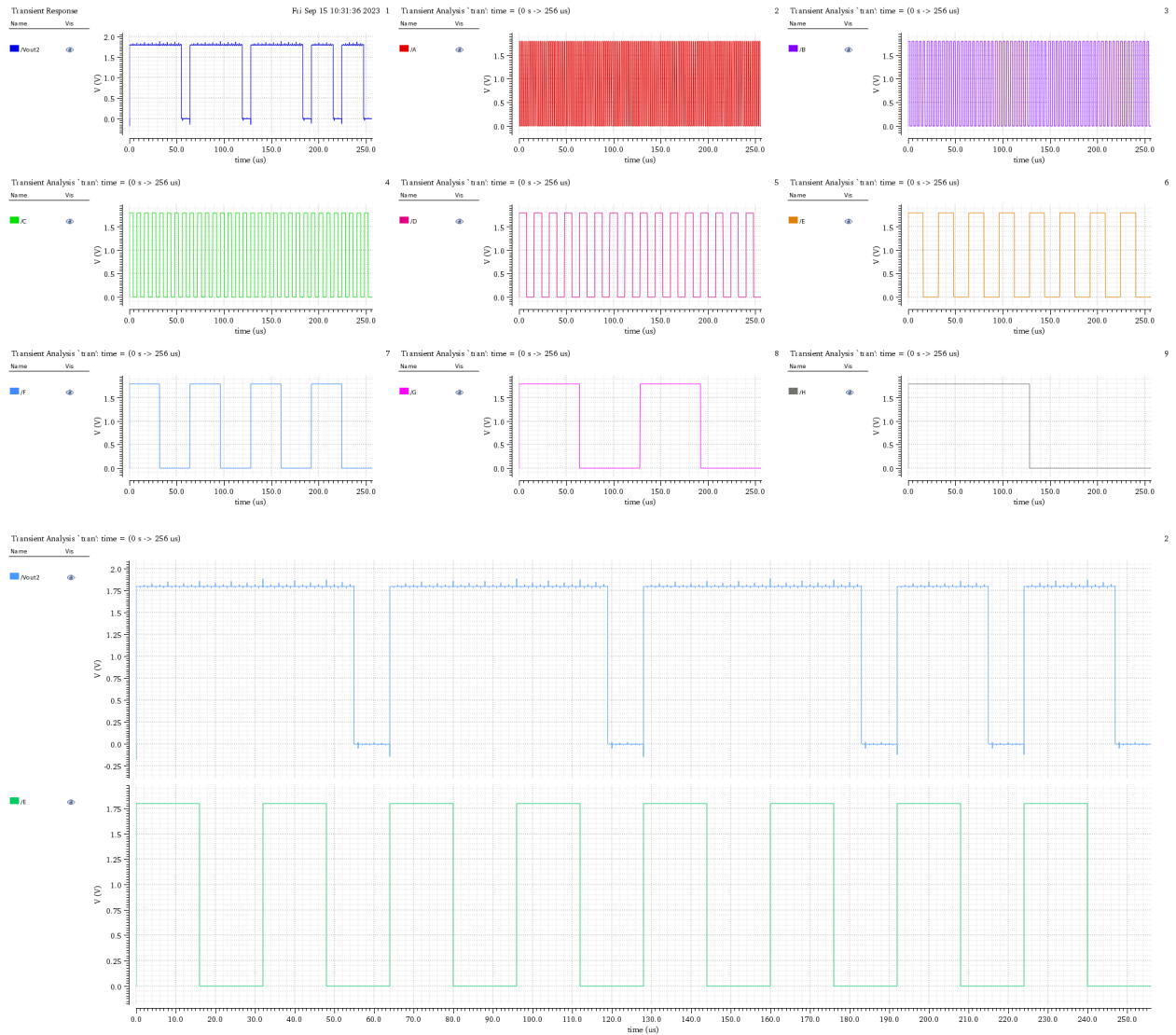

When E = HIGH, Vout2 = HIGH as expected!

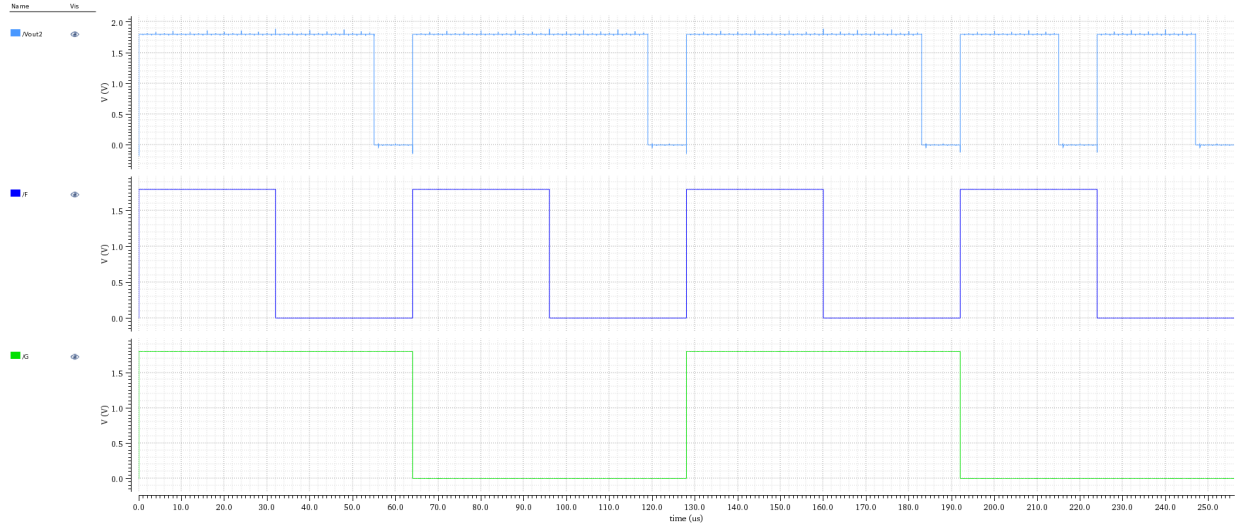


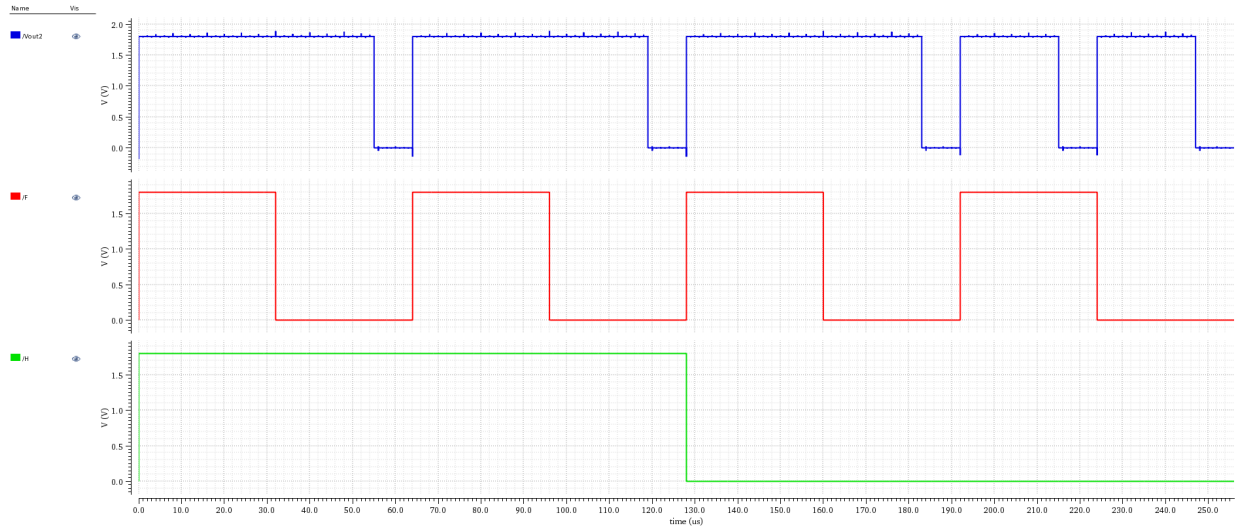When (F & G) = HIGH, Vout2 = HIGH as expected!



When (F & H) = HIGH, Vout2 = HIGH as expected!

Schematic-2:

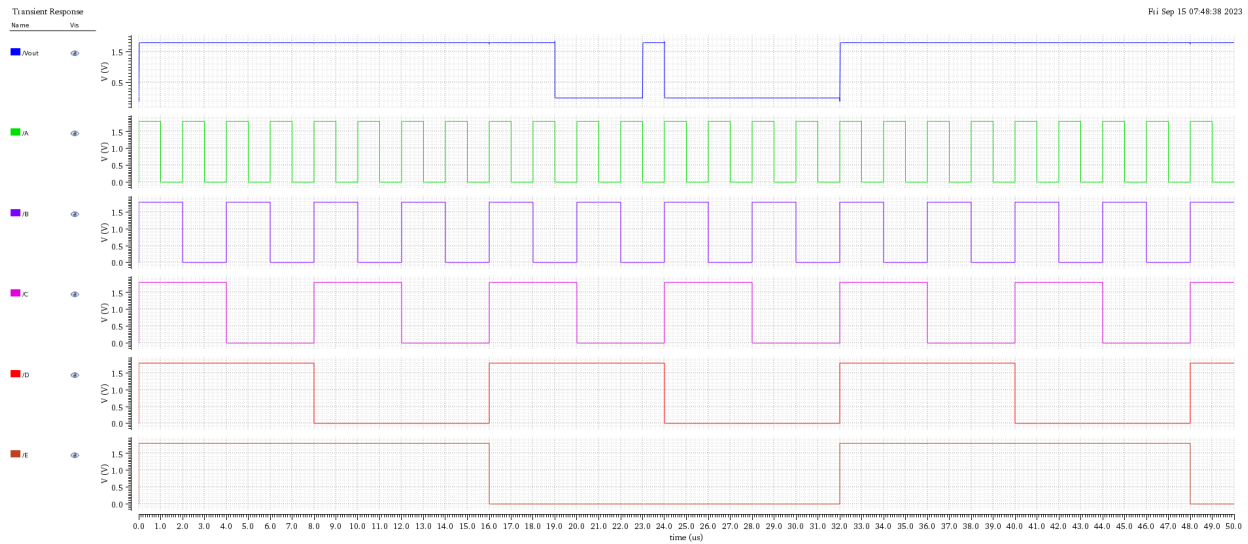

- When $E = \text{HIGH}$, $V_{\text{out}} = \text{HIGH}$ as expected!
- If we find out the response of $[(A + B)' \wedge C].D$, we 'll get the range of values of the output “ V_{out} ” = HIGH that are not compensated by taking $E = \text{HIGH}$ alone.

Conclusion:

In this experiment, we learnt how to design combinational logic circuits using Static CMOS Logic. In particular, we have also looked into the fact that **increasing the fan-in of CMOS circuits leads to higher delays** because the **resistance of the RC network increases**. This will not be the case with **cascading two/more sublogic functions** to implement the original function.