

Exercise 8

1. Design a dynamic race-free cascaded structure for the following Boolean function:

$$X = [(AB + C) D']'$$

$$Y = X + EF'$$