

Experiment 8

CMOS Layout Design

1. Design a CMOS inverter with equal PMOS and NMOS widths (400 nm). Create a layout of the same inverter.
2. Check the design rules and verify the layout of the inverter with its schematic.