

## Experiment 9

### Dynamic Logic Design

1. Design a dynamic CMOS circuit for the following Boolean equations.

(a)  $X = (AB) + C + (DE) + F + G(BC)$

(b)  $Y = [((AB)' \wedge C) + D] E$