

Exercise 3

1. Design a static CMOS circuit for the following Boolean equations.

a) $Y = (A+B+C) D + E + F (G+H)$

b) $Z = [((A+B)' \wedge C) D] + E$