

Experiment 6

Combinational Logic Design

1. Design a 2-input AND gate, 2-input OR gate, and 2-input XOR gate using both pass transistor logic and transmission gate logic.
2. Calculate the power dissipation, delay, and voltage swing of all the gates in (1) and compare them with the respective gates in experiment 4. Comment on your observations.