

## VLSI LAB Exercise-8 NORA Logic


Group Number: 2

Group Members:


Thathapudi Sanjeev Paul Joel - 2020AAPS0120H


Aditya Anirudh - 2020AAPS0373H

Design Workout:

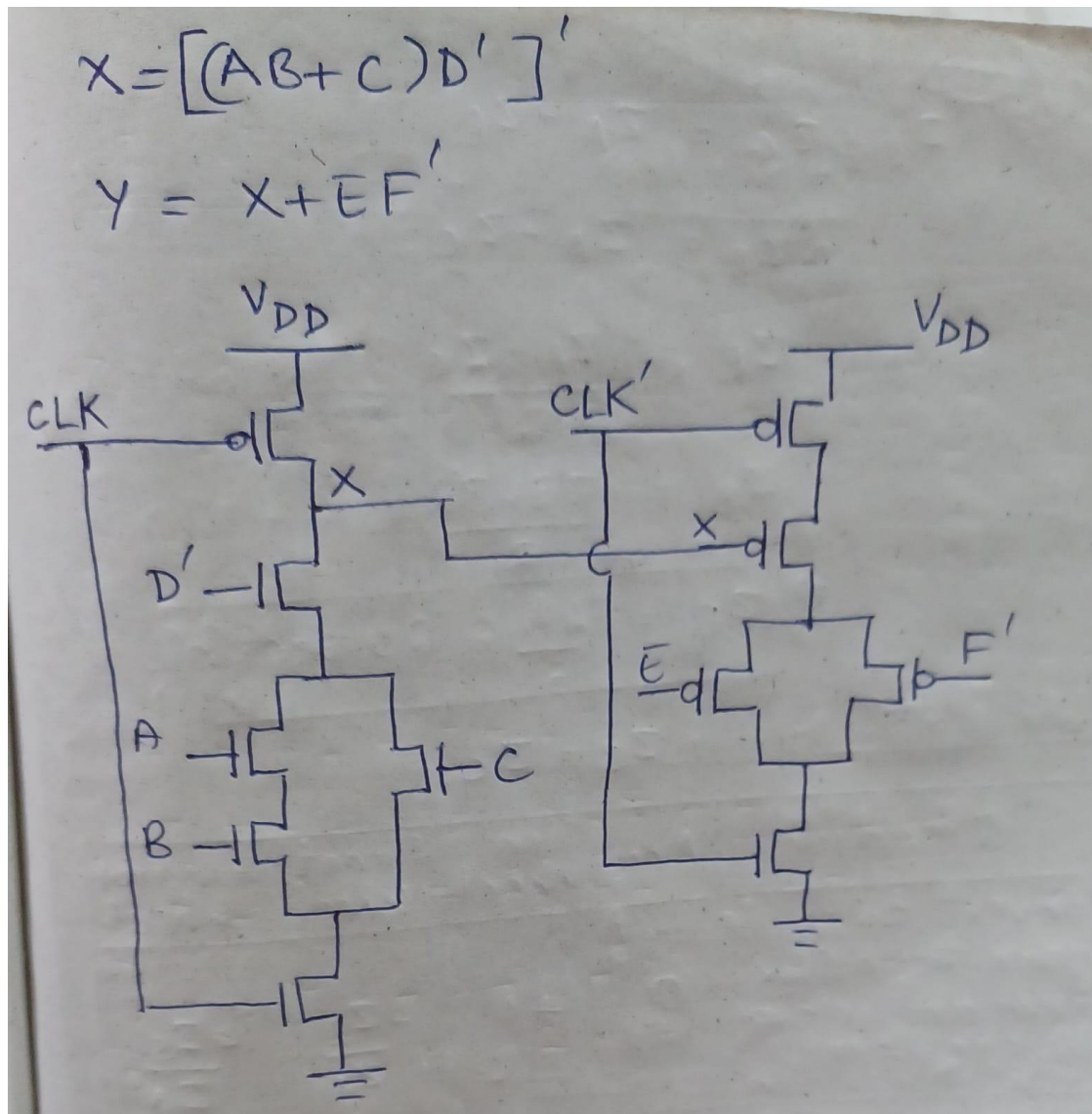


Giving pulse excitations:-

 

 


Fri Oct 27 16:58:26 2023 1

A = 1, B = 1, C = 0, D = 0, E = 1, F = 1

 

Fri Oct 27 16:54:12 2023 1

A = 1, B = 1, C = 0, D = 1, E = 1, F = 1

 

### Inferences:

1.  $V_{out} = 1.8 \text{ V}$ , whenever  $CLK = 0$ , because the **2<sup>nd</sup> stage is in the pre-discharge phase** in this period.
2. Three cases have been depicted while giving constant input excitations to the above circuit:
  - a. The 1<sup>st</sup> stage is evaluated while the 2<sup>nd</sup> stage is not.
  - b. Both the stages are evaluated.
  - c. Both the stages are not evaluated.
3. While designing the NMOS and PMOS logic blocks, we have to ensure that, the **race condition for inputs is avoided** by **giving the input non-inverted to the second stage** as PMOS transistors are ON only when  $V_{in} = \text{LOW}$ , while the NMOS stage is initially pre-charged and not pre-discharged.

### Conclusion:

In this experiment, we designed a combinational circuit by **cascading two stages of dynamic logic**: one using NMOS logic while the other using PMOS logic for the evaluation phase. This ensures that the **race condition is avoided (NORA Logic)**.