

# **VLSI DESIGN LAB Experiment-3 CMOS INVERTER (Part-2)**

Group Number: 2

Group Members:

Thathapudi Sanjeev Paul Joel - 2020AAPS0120H

Aditya Anirudh - 2020AAPS0373H

Width of PMOS transistor when  $V_M = 0.8$  V:

## CMOS INVERTER-2

At the midpoint voltage,  $V_{in} = V_{out} = V_M$ , and both NMOS and PMOS are in saturation,

$$\Rightarrow I_{DS, n} = I_{DS, p}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n (V_{in} - V_{T0, n})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{in} - V_{DD} - V_{T0, p})^2$$

$$\Rightarrow \frac{(W/L)_n}{(W/L)_p} = \frac{\mu_p}{\mu_n} \cdot \frac{(V_{in} - V_{DD} - V_{T0, p})^2}{(V_{in} - V_{T0, n})^2}$$

$$\Rightarrow (W/L)_p = \frac{\mu_n}{\mu_p} \cdot \frac{(V_{in} - V_{T0, n})^2}{(V_{in} - V_{DD} - V_{T0, p})^2} \cdot (W/L)_n$$

$$\therefore \frac{\mu_n}{\mu_p} = \frac{\mu_n C_{ox}}{\mu_p C_{ox}} = \frac{350}{70} = 5, V_M = 0.8V = V_{in},$$

$$V_{T0, n} = 0.429V, V_{T0, p} = -0.468V.$$

substituting these values, we get -

$$\frac{(W/L)_p}{(W/L)_n} = 5 \cdot \frac{(0.8 - 0.429)^2}{(0.8 - 1.8 + 0.468)^2}$$

$$\therefore \underline{L_p = L_n}$$

$$\Rightarrow \frac{W_p}{W_n} = 2.432$$


Taking  $W_n = 400 \text{ nm}$ , we get  $W_p$  as -

$$W_p = 2.432 \times 400 = 972.8 \approx 970 \text{ nm}$$


$$\Rightarrow \boxed{W_p = 970 \text{ nm}} \rightarrow \text{For } V_M = 0.8V$$

### Schematics:

CMOS Inverter with  $V_M = 0.8$  V:

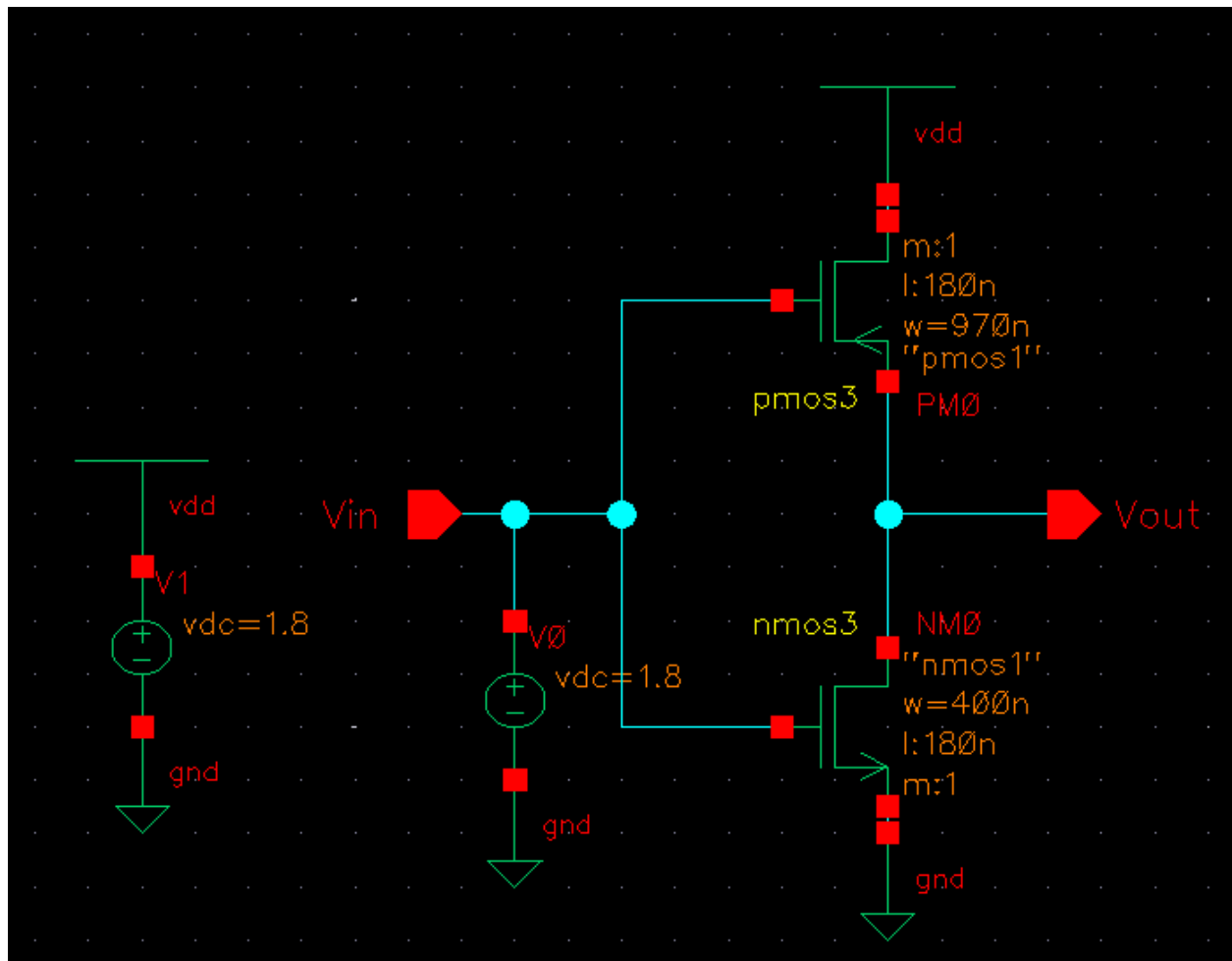


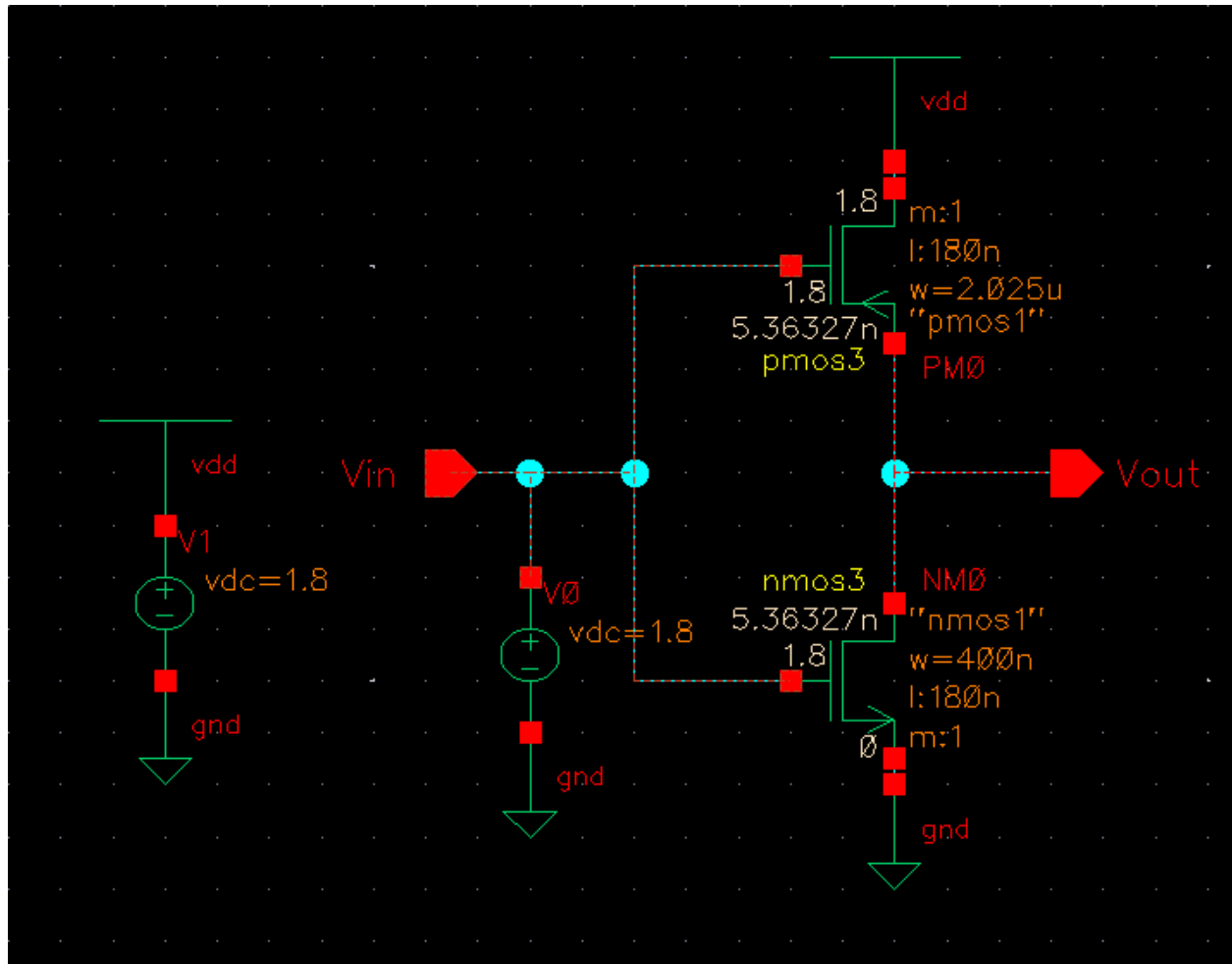CMOS Inverter with  $V_M = 0.9$  V (Symmetric switching threshold):




## Waveforms:

CMOS Inverter with  $V_M = 0.8$  V:

 

 *Plot displaying the switching threshold at nearly  $V_M = 0.81$  V.*




*Plot displaying the derivative,  $dV_{out}/dV_{in}$ . The points where the ordinate = -1 are also displayed.*




*Plot displaying the ordered pairs,  $(V_{IL}, V_{OH})$  &  $(V_{IH}, V_{OL})$ .*

 
CMOS Inverter with  $V_M = 0.9$  V (Symmetric switching threshold):



 Plot displaying the switching threshold at nearly  $V_M = 0.9$  V.



 Plot displaying the derivative,  $dV_{out}/dV_{in}$ . The points where the ordinate = -1 are also displayed.



*Plot displaying the ordered pairs,  $(V_{IL}, V_{OH})$  &  $(V_{IH}, V_{OL})$ .*

### Metrics Measured:

CMOS Inverter with  $V_M = 0.8$  V:

$V_M = 809.578$  mV (practical)

$V_{IL} = 650.3584$  mV

$V_{IH} = 944.4542$  mV

$V_{OL} = 95.80754$  mV

$V_{OH} = 1.67637$  V

$NM_H = 0.731916$  V

$NM_L = 0.55455$  V

$W_p/W_n = 2.432$  (For obtaining  $V_M = 0.8$  V)

$W_p \sim 970$  nm for  $W_n = 400$  nm.

CMOS Inverter with  $V_M = 0.9$  V (Symmetric switching threshold):

$V_M = 712.09$  mV

$V_{IL} = 776.175$  mV

$V_{IH} = 1.04933$  V

$V_{OL} = 83.2004$  mV

$V_{OH} = 1.64816$  V

$NM_H = 0.59883$  V

$NM_L = 0.6929746$  V

$W_p/W_n = 5.0625$  (For symmetrical transfer characteristics)

$W_p \sim 2.025$   $\mu$ m for  $W_n = 400$  nm.

The noise margin of output = logic-0 increased for  $V_M = 0.9 \text{ V}$  as compared to  $V_M = 0.8 \text{ V}$ . This is expected because even when we assume that the transition is abrupt ( $V_{IL} = V_{IH} = V_M$ ), increasing  $V_M$  from 0.8 to 0.9 V would increase the range of voltages where input = logic-0. Similarly, this would decrease the range of voltages where input = logic-1 and hence the noise margin of output = logic-1 is reduced.

For simplicity, assuming  $V_{IL} = V_{IH} = V_M$  and  $V_{OL} = 0$ ,  $V_{OH} = V_{DD} = 1.8 \text{ V}$ :

$$V_M = 0.8 \text{ V},$$

$$NM_H = V_{OH} - V_{IH} = 1.8 - 0.8 = 1.0 \text{ V}$$

$$NM_L = V_{IL} - V_{OL} = 0.8 - 0 = 0.8 \text{ V}$$

$$V_M = 0.9 \text{ V (increased } V_M),$$

$$NM_H = V_{OH} - V_{IH} = 1.8 - 0.9 = 0.9 \text{ V (HIGH Noise Margin reduced)}$$

$$NM_L = V_{IL} - V_{OL} = 0.9 - 0 = 0.9 \text{ V (LOW Noise Margin increased)}$$

### Conclusion:

In this experiment, we designed a CMOS Inverter with a custom switching threshold ( $V_M = 0.8 \text{ V}$ ). We have obtained the  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$ ,  $V_{OH}$  values, and the noise margins  $NM_L$ , &  $NM_H$ . Finally, we also obtained the same parameters for a CMOS inverter with a symmetric switching threshold and compared its performance with that of  $V_M = 0.8 \text{ V}$ .