

Exercise 7

1. Design a NAND gate and create a layout of the same.
2. Check the design rules and verify the layout of the NAND gate with its schematic.